

**Final Projects**  
**Course**  
**Electronic Circuit Design Technology (ECDT)**

**Marking criteria:**

**Total marks are 100**

**Each Project has three parts:**

- **Part (i) has 20 marks**
- **Part (ii) has 35 marks**
- **Part (iii) has 45 marks**

## Project # 1


### Group members:

潘盈盈 Pan Yingying 2019329600060

张紫怡 Zhang Ziyi 2019329600091

王茜 Wang Xi 2019329600090

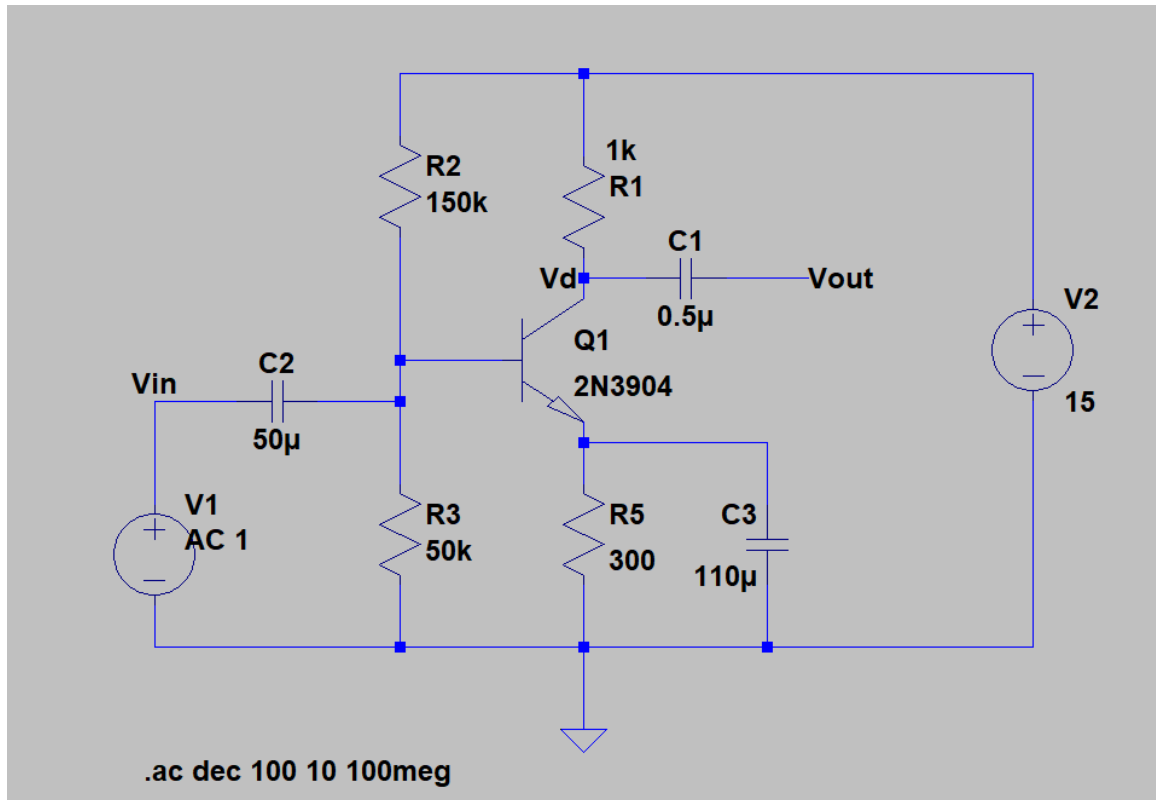- Do the** Mathematical Analysis i.e. DC and Small signal analysis of the amplifier shown in figure and find the voltage gain (Reference class lecture #1)
- Simulate the circuit in LTSpice and plot the Gain in dB and Linear scale, find the 3db bandwidth (Reference class lecture #1)
- Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)


## Project # 2

### Group members:

许贤伟 Xu Xianwei 2019329600023

童佳恩 Tong Jiaen2019329600081

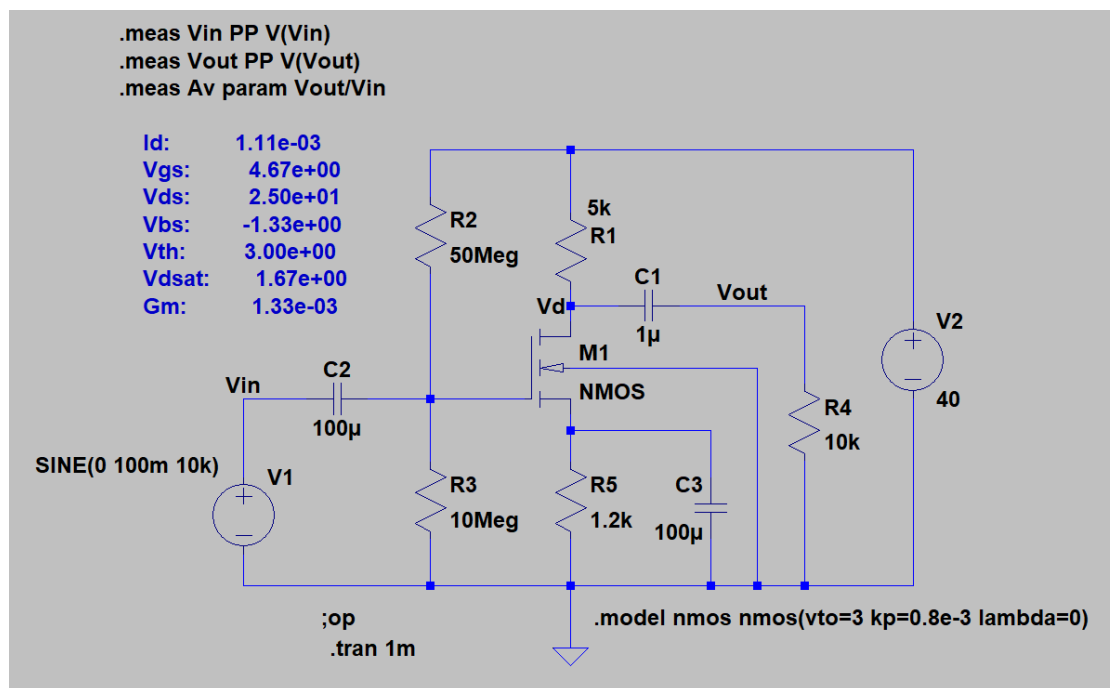- i. Do the Mathematical Analysis i.e. DC and Small signal analysis of the MOSFET amplifier shown in figure and find the voltage gain (Reference class lecture #2 & 3)
- ii. Simulate the circuit in LTSpice and plot the Gain in dB and Linear scale, find the 3db bandwidth (Reference class lecture #2 & 3)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)


## Project # 3

### Group members:

张静茹 Zhang Jingru 2019327100043

柯玲 Ke Ling 2019339902122

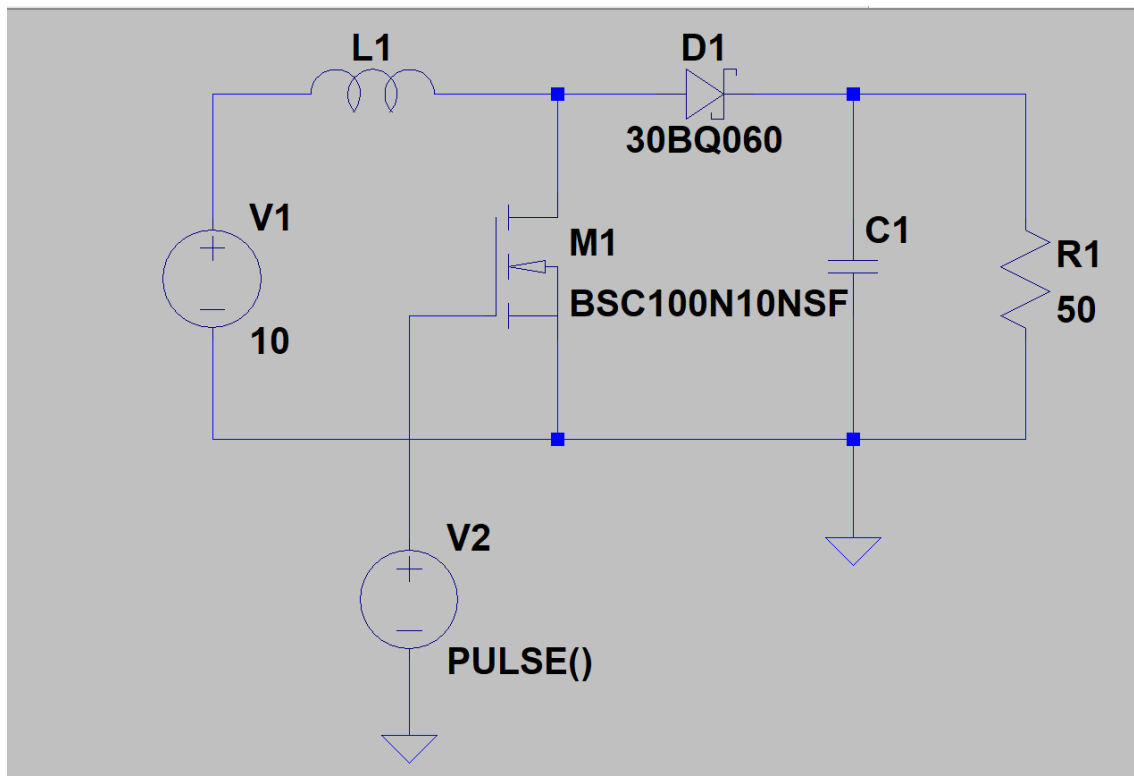- i. Design a boost converter that will have an output of 40 V from a 10-V source. Design for continuous inductor current and an output ripple voltage of less than one percent. The load is a resistance of 50 . Assume ideal components for this design.
- ii. Simulate the circuit in LTSpice and plot the inductor current, capacitor current, output voltage and the switching signal(Reference class lecture #5 & 6)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 4


Group members:

魏文桐 Wei Wentong 2019329600137

汪跃俊 Wang Yuejun 2019329600134

黎晓航 Li Xiaohang 2019329600129

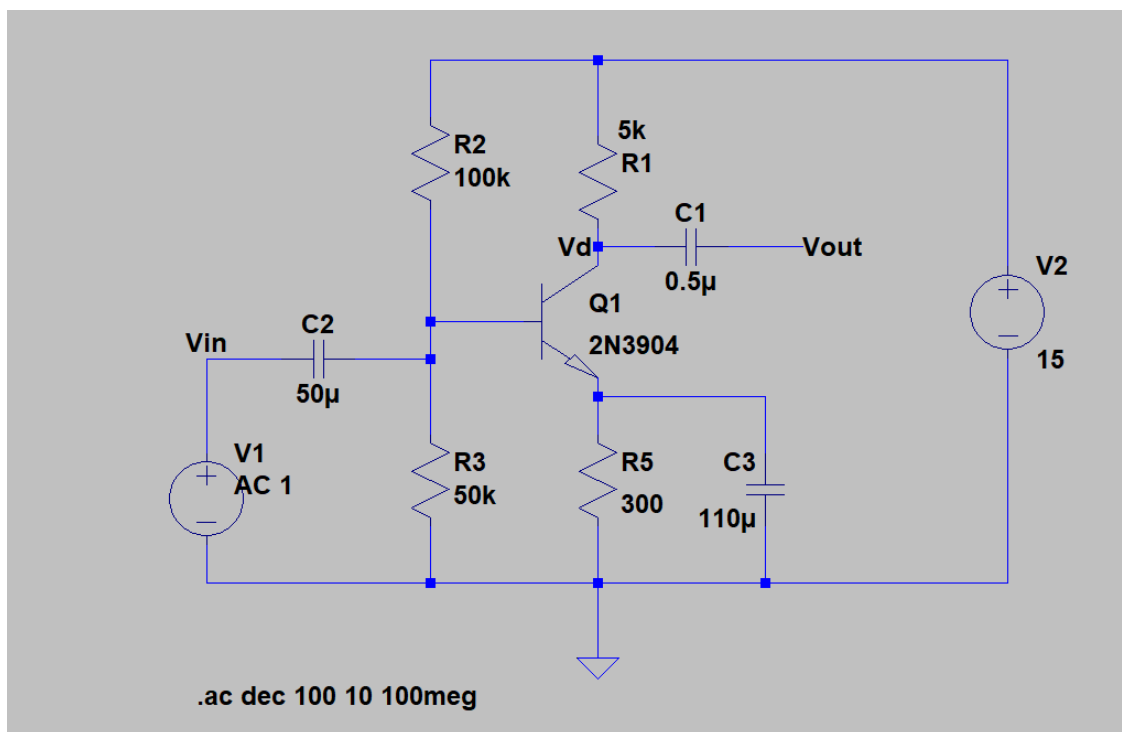- i. **Do the** Mathematical Analysis i.e. DC and Small signal analysis of the amplifier shown in figure and find the voltage gain (Reference class lecture #1)
- ii. Simulate the circuit in LTSpice and plot the Gain in dB and Linear scale, find the 3db bandwidth (Reference class lecture #1)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 5


### Group members:

陈宇宁 Chen Yunning 2019329600123

蒋振豪 Jiang Zhenhao 2019329600127

史君豪 Shi Junhao 2019330300058

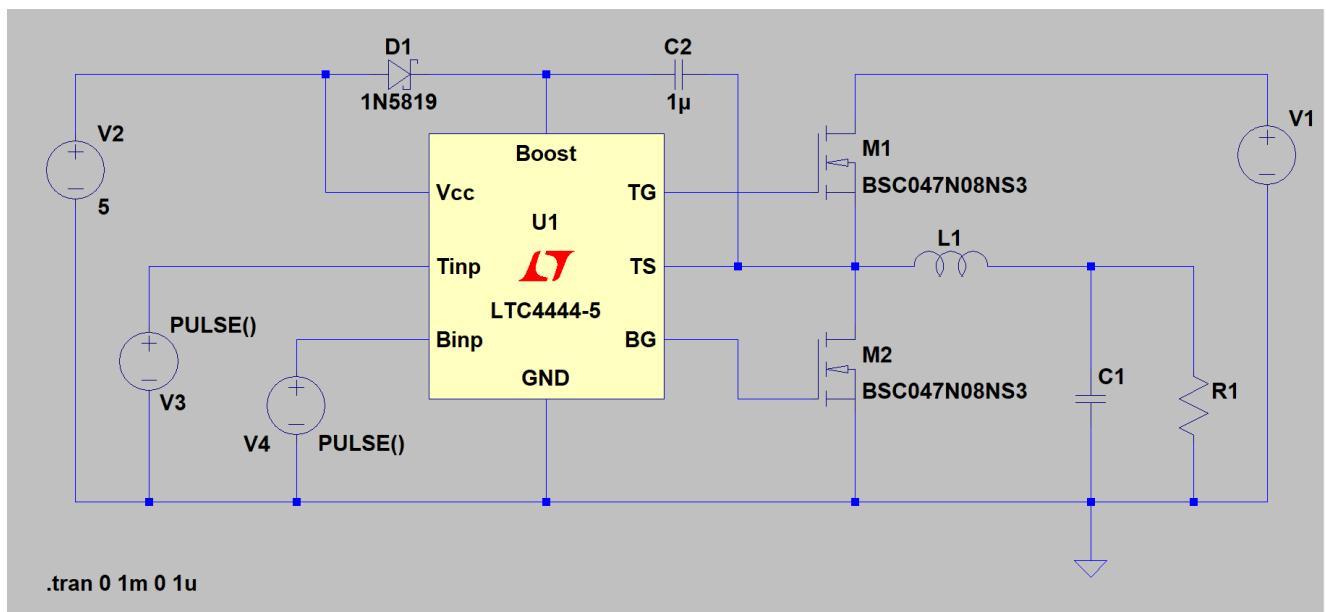- i. Design a buck converter  $V_{in}$  ( $V_1$ ) = 40V and  $V_{out}$  = 20V, Load Current is 1A, inductor current variation is 40% of load current and operating frequency is 100kHz
- ii. Simulate the circuit in LTSpice and plot the inductor current, capacitor current, output voltage and the switching signal(Reference class lecture #5 & 6)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 6

### Group members:


李成杯 LiChengBei 2019329600044

程坤 ChengKun 2019329600006

Design an Astable Multivibrator circuit shown in Figure below and generate a square wave with frequency of 500 kHz (Please refer to Lecture 8 (video lecture)).

The project report will be composed on the following steps

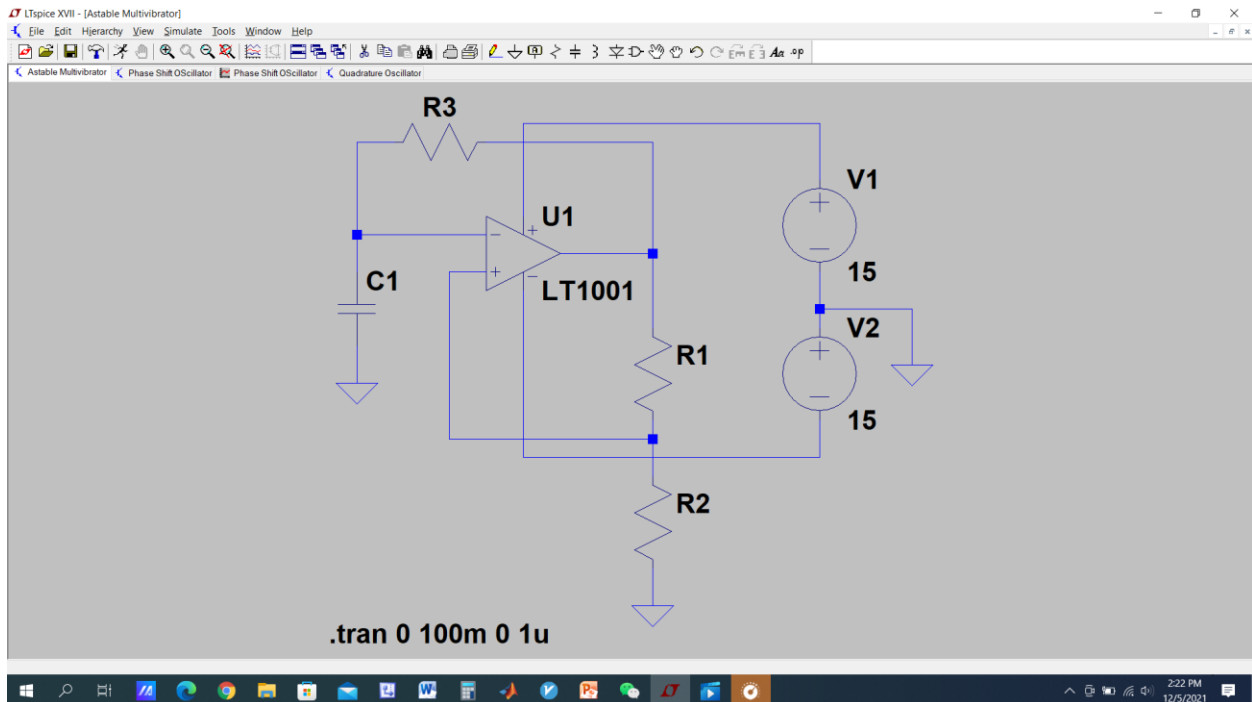- i. Mathematical Analysis
- ii. Simulate the circuit in LTSpice
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)


## Project # 7

Group members:

吴子山 Wu Zishan 2019329600004

陈星海 Chen Xinghai 2019330300270

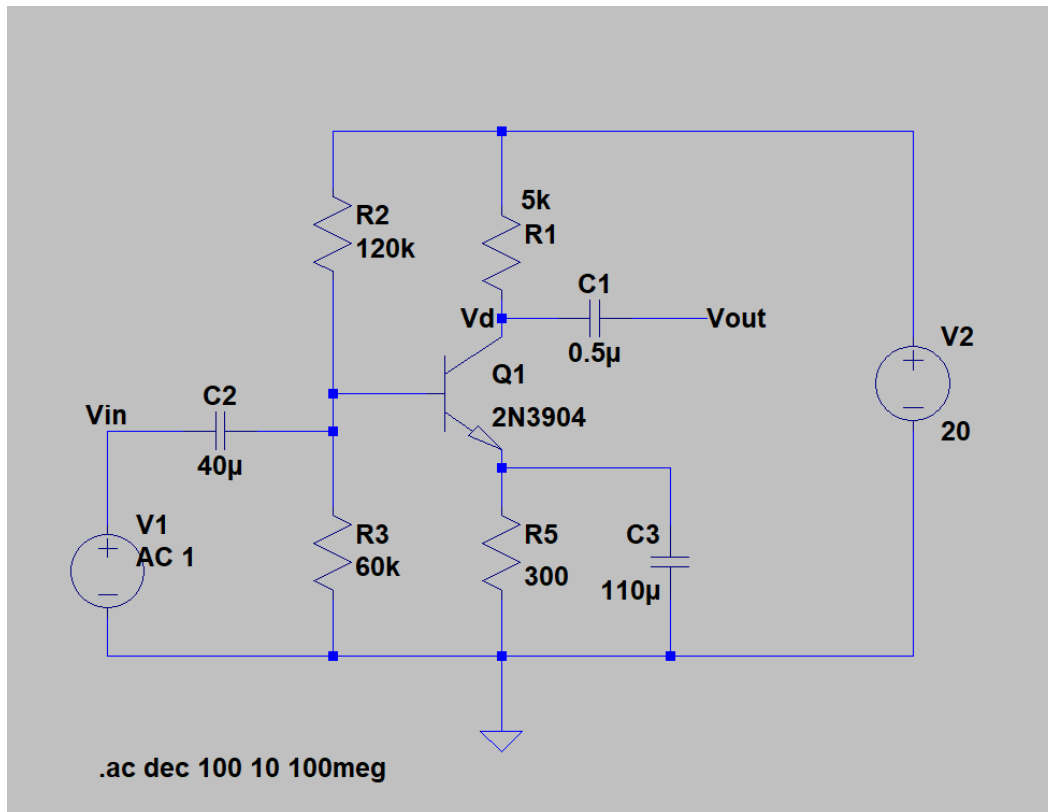- i. **Do the** Mathematical Analysis i.e. DC and Small signal analysis of the amplifier shown in figure and find the voltage gain (Reference class lecture #1)
- ii. Simulate the circuit in LTSpice and plot the Gain in dB and Linear scale, find the 3db bandwidth (Reference class lecture #1)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)



## Project # 8


### Group members:

王温杰 Wang Wenjie 2019329600104

郭一 Guo Yi 2019329600039

赵景森 Zhao Jingsen 2019329600115

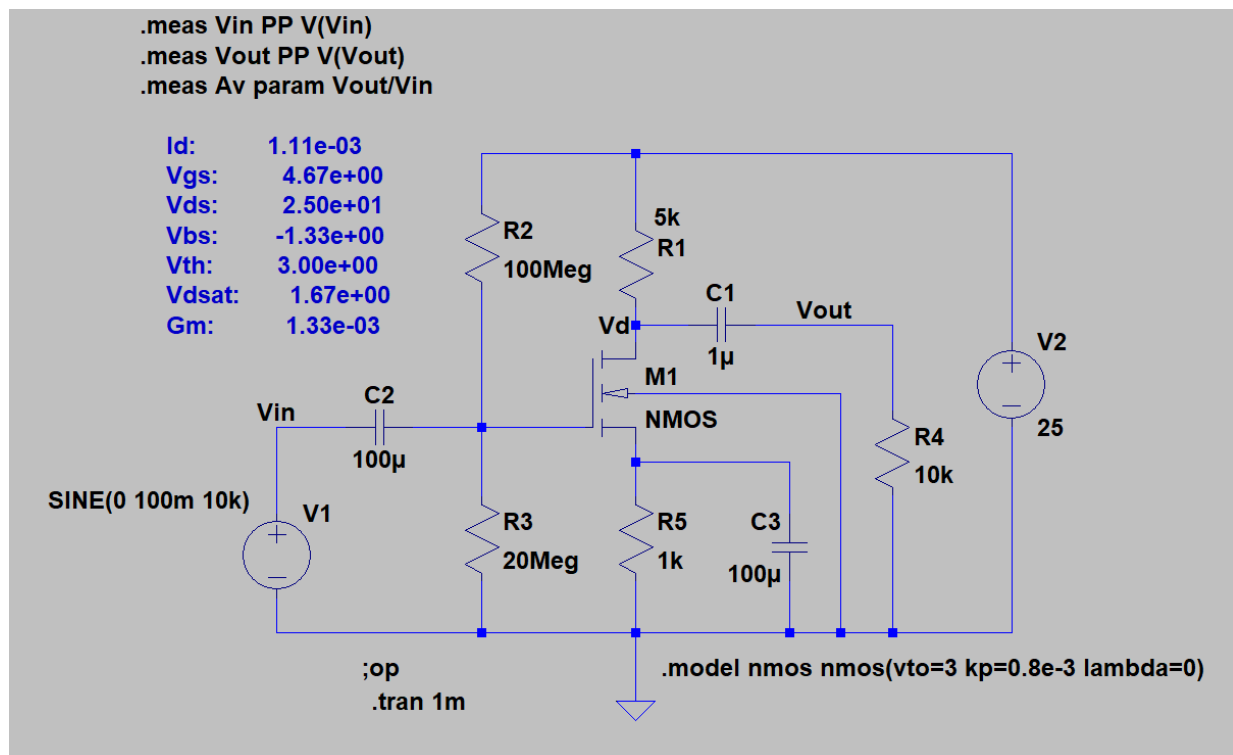- i. Do the Mathematical Analysis i.e. DC and Small signal analysis of the MOSFET amplifier shown in figure and find the voltage gain (Reference class lecture #2 & 3)
- ii. Simulate the circuit in LTSpice and plot the Gain in dB and Linear scale, find the 3db bandwidth (Reference class lecture #2 & 3)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 9


### Group members:

杨涵 Yang Han 2019329600138

王宇航 Wang Yuhang 2019329600136

张辰宇 Zhang Chenyu 2019329600054

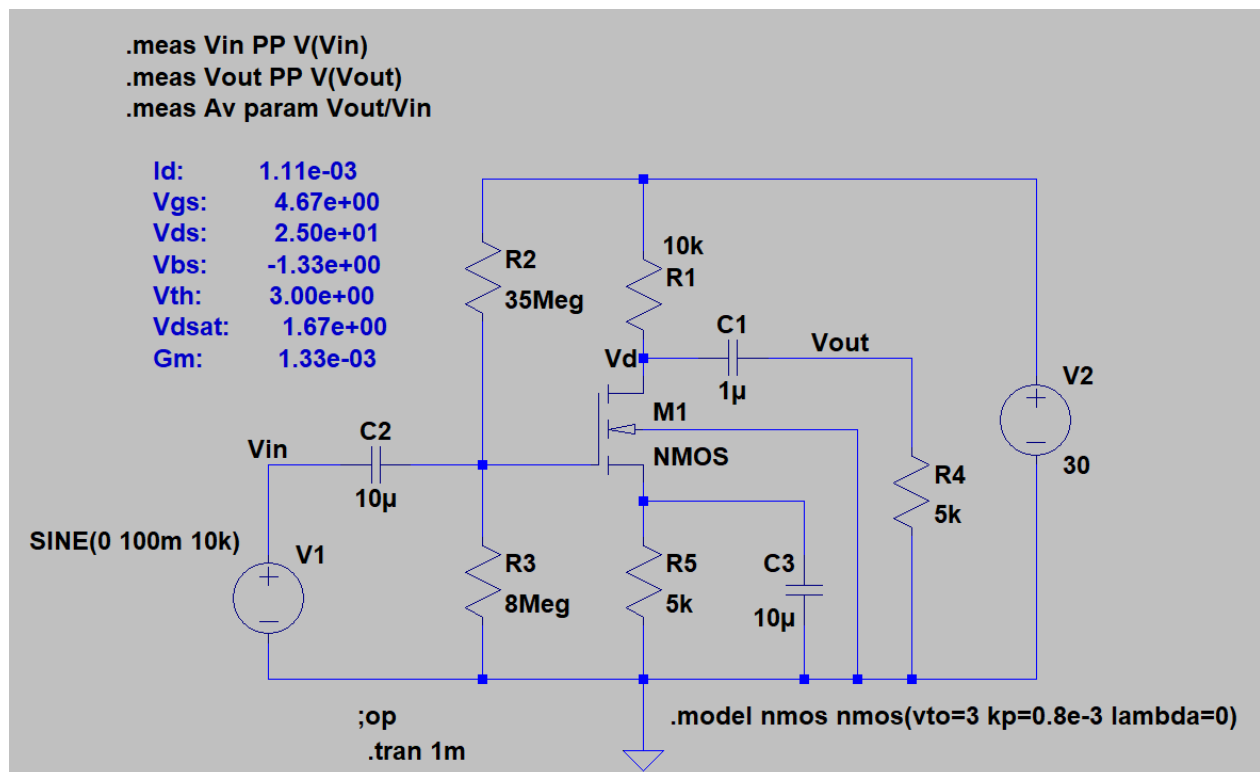- i. Do the Mathematical Analysis i.e. DC and Small signal analysis of the MOSFET amplifier shown in figure and find the voltage gain (Reference class lecture #2 & 3)
- ii. Simulate the circuit in LTSpice and plot the Gain in dB and Linear scale, find the 3db bandwidth (Reference class lecture #2 & 3)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)


## Project # 10

### Group members:

杨晨乾 Yang Chenqian 2019329600052

郑嘉琪 Zheng Jiaqi 2019329600057

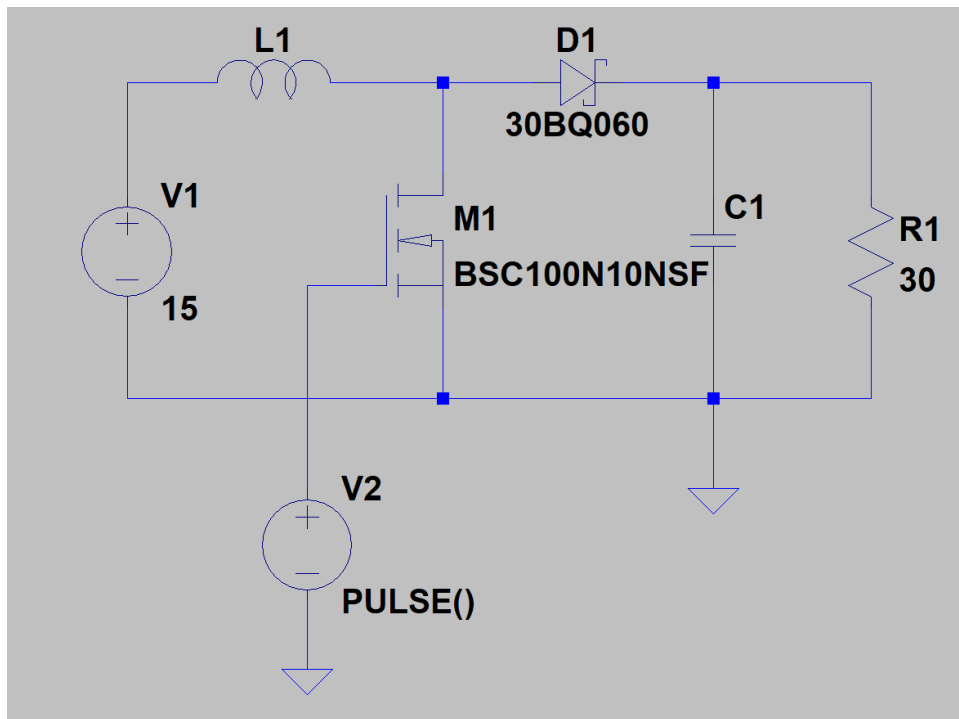- i. Design a boost converter that will have an output of 45 V from a 15-V source. Design for continuous inductor current and an output ripple voltage of less than one percent. The load is a resistance of 30-Ohm. Assume ideal components for this design.
- ii. Simulate the circuit in LTSpice and plot the inductor current, capacitor current, output voltage and the switching signal(Reference class lecture #5 & 6)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 11

### Group members:


葛良旺 Ge Liangwang 2019329600038

王玉 Wang Yu 2019329600050

Design and mathematically a Phase shift oscillator generating a frequency of 250 kHz (Please refer to Lecture 7 (video lecture)).

The project report will be composed on the following steps

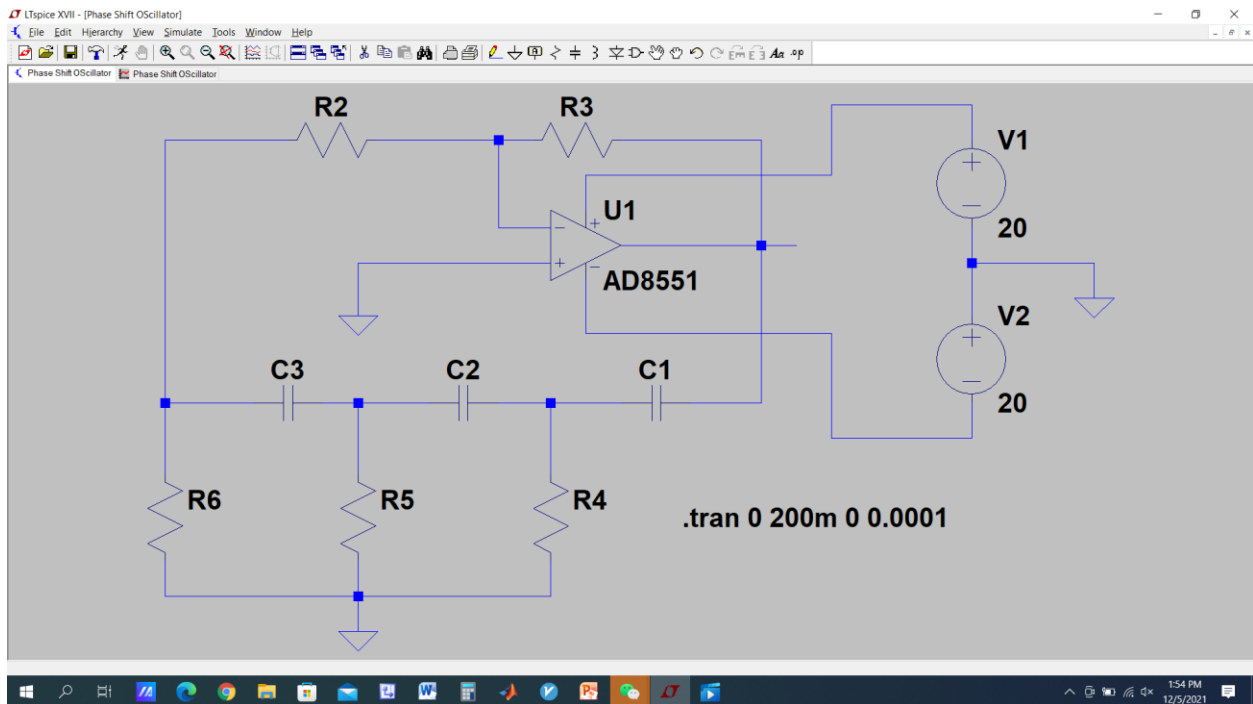- i. Mathematical Analysis
- ii. Simulate the circuit in LTSpice
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 12


### Group members:

陈天霖 Chen Tianlin 2019329600035

张志远 Zhangzhiyuan 2019329600055

阚昊宇 Kan Haoyu 2019329600128

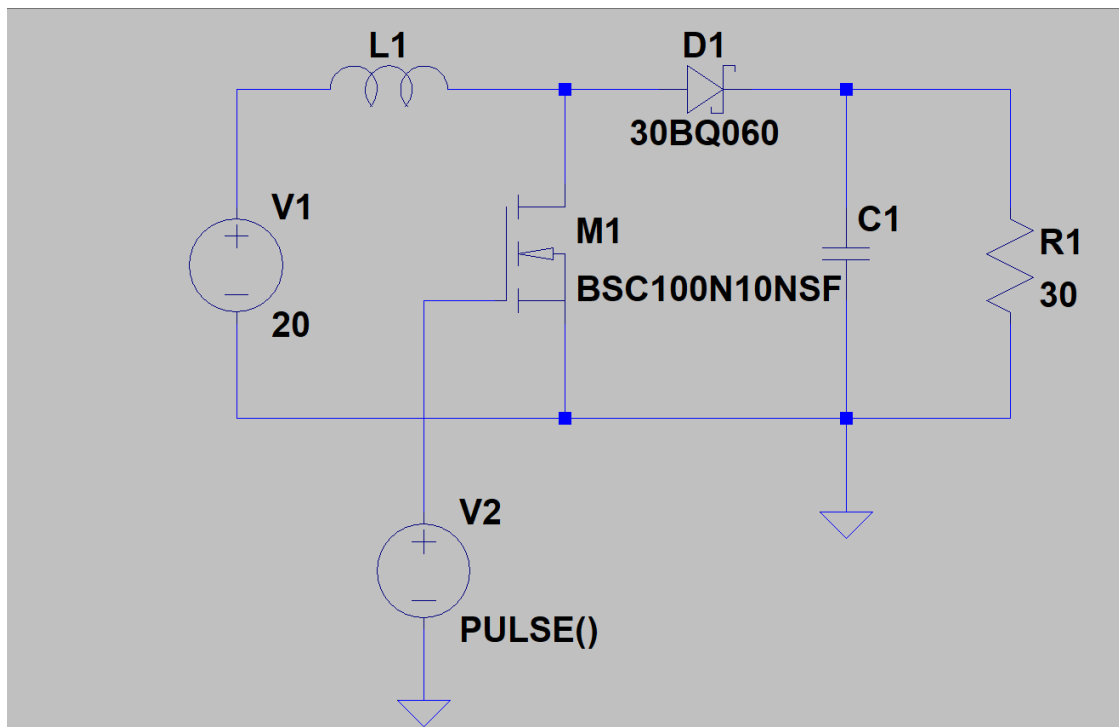- i. Design a boost converter that will have an output of 60 V from a 20V source. Design for continuous inductor current and an output ripple voltage of less than one percent. The load is a resistance of 30-Ohm. Assume ideal components for this design.
- ii. Simulate the circuit in LTSpice and plot the inductor current, capacitor current, output voltage and the switching signal(Reference class lecture #5 & 6)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 13


Group members:

李博 Li Bo 2019330361015

徐誉宁 Xu Yuning 2019329600109

叶毅 Ye Yi 2019329600111

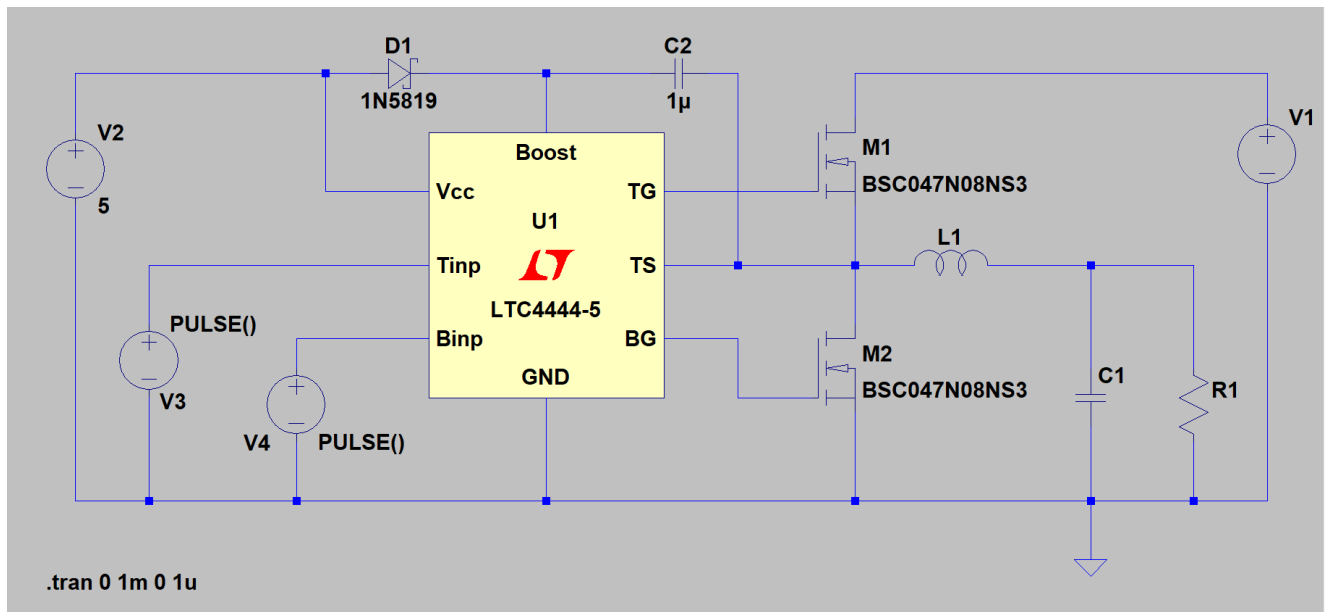- i. Design a buck converter  $V_{in}$  ( $V_1$ ) = 50V and  $V_{out}$  = 10V, Load Current is 1A, inductor current variation is 30% of load current and operating frequency is 150kHz
- ii. Simulate the circuit in LTSpice and plot the inductor current, capacitor current, output voltage and the switching signal(Reference class lecture #5 & 6)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 14

**Group members:**


**胡逸飞 Hu Yifei 2019337261145**

**康健雄 Kang Jianxiong 2019327100083**

Design and mathematically a Wein-Bridge oscillator generating a frequency of 100 kHz (Please refer to Lecture 7 (video lecture)).

The project report will be composed on the following steps

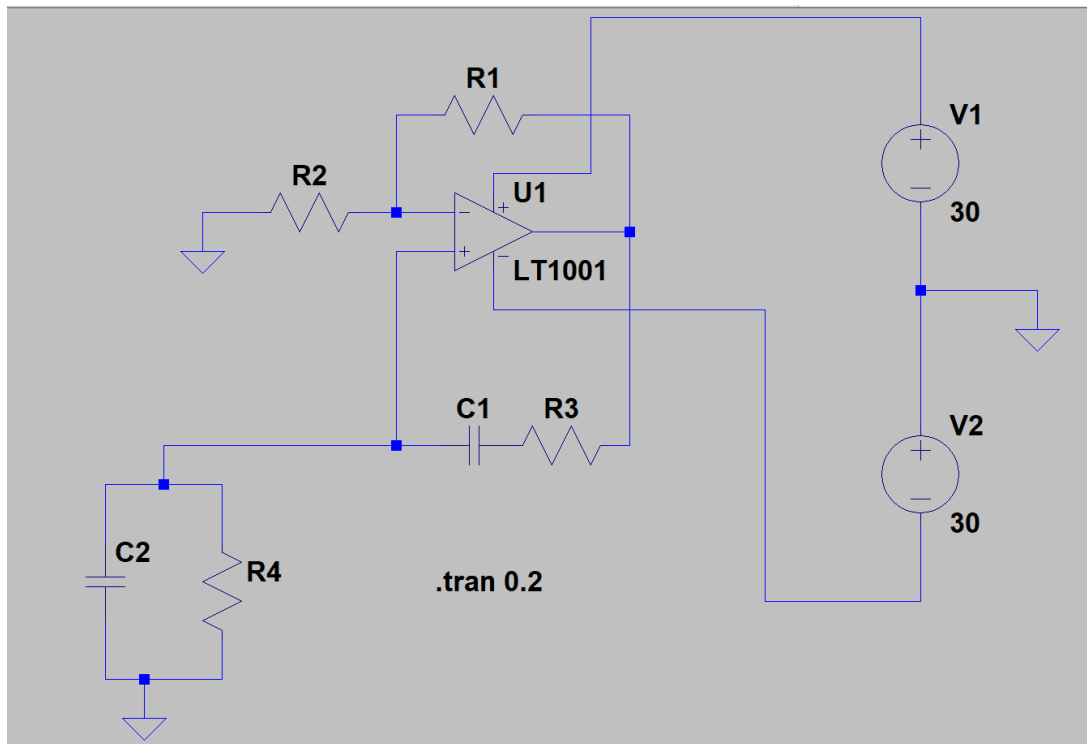- i. Mathematical Analysis
- ii. Simulate the circuit in LTSpice
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 15


Group members:

方世纪 Fang Shiji 2019329600094

樊星 Fan Xing 2019329600093

刘以凡 Liu Yifan 2019329600099

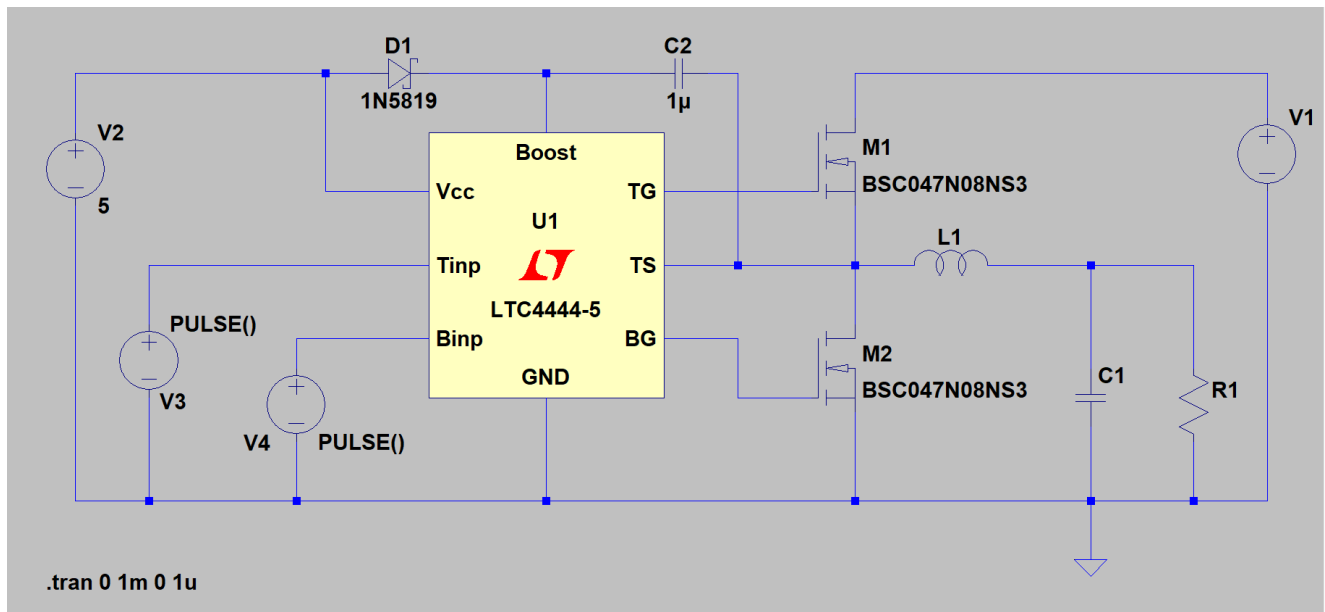- i. Design a buck converter  $V_{in}$  ( $V_1$ ) = 70V and  $V_{out}$  = 40V, Load Current is 1.5A, inductor current variation is 35% of load current and operating frequency is 250kHz
- ii. Simulate the circuit in LTSpice and plot the inductor current, capacitor current, output voltage and the switching signal(Reference class lecture #5 & 6)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)



## Project # 16

### Group members:

李志豪 Li zhihao 2019329600097


张海丰 Zhang haifeng 2019329600114

戴晶峰 Dai Jingfeng 2019329600037

Design and mathematically a quadrature oscillator generating a frequency of 100 kHz (Please refer to Lecture 8 (video lecture)).

The project report will be composed on the following steps

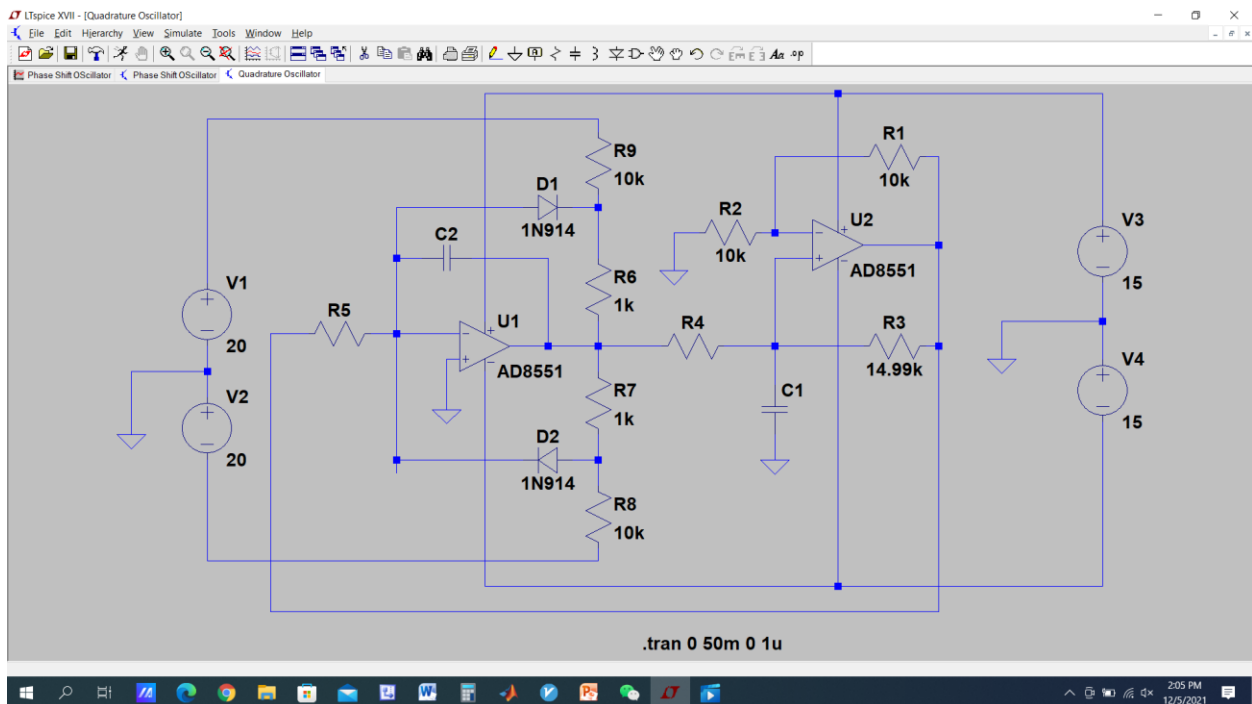- i. Mathematical Analysis
- ii. Simulate the circuit in LTSpice
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 17


Group members:

过泽栋 Guo Zedong 2019331201019

张振洋 Zhang Zhenyang 2019329600142

蒋武鹏 Jiang Wupeng 2019327130014

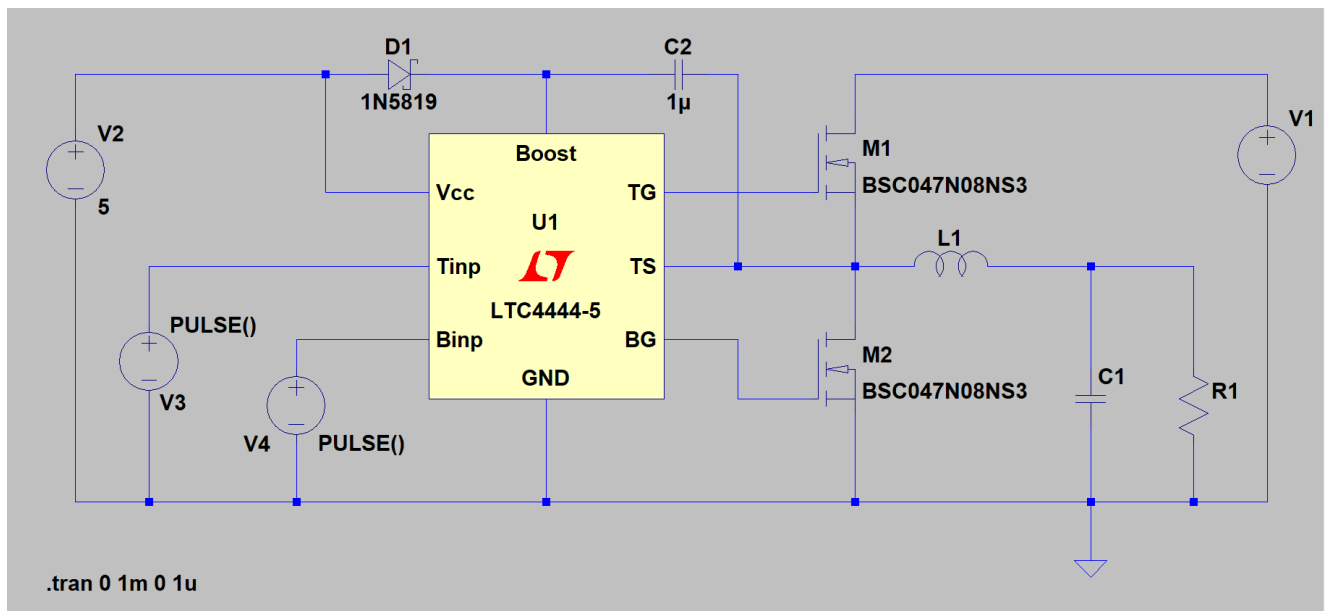- i. Design a buck converter  $V_{in}$  ( $V_1$ ) = 30V and  $V_{out}$  = 10V, Load Current is 2.5A, inductor current variation is 35% of load current and operating frequency is 300kHz
- ii. Simulate the circuit in LTSpice and plot the inductor current, capacitor current, output voltage and the switching signal(Reference class lecture #5 & 6)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 18

Group members:

尤彦辰 You Yanchen2019330300226


金飞宇 Jin Feiyu2019329600096

叶俊龙 Ye Junlong2019329600110

Design and mathematically a Wein-Bridge oscillator generating a frequency of 50kHz (Please refer to Lecture 7 (video lecture))

The project report will be composed on the following steps

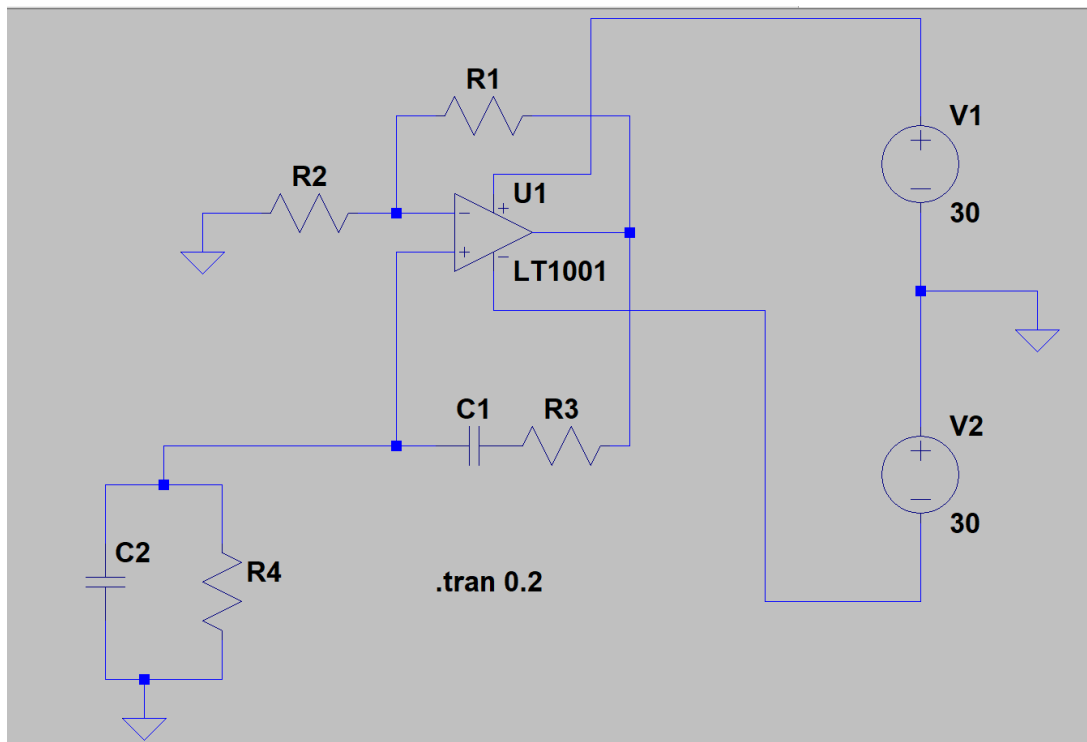- i. Mathematical Analysis
- ii. Simulate the circuit in LTSpice
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 19

### Group members:


吕润年 Lv Runnian 2019339901050

陆云昊 Lu Yunhao 2019339901049

Design and mathematically a Phase shift oscillator generating a frequency of 500 kHz (Please refer to Lecture 7 (video lecture)).

The project report will be composed on the following steps

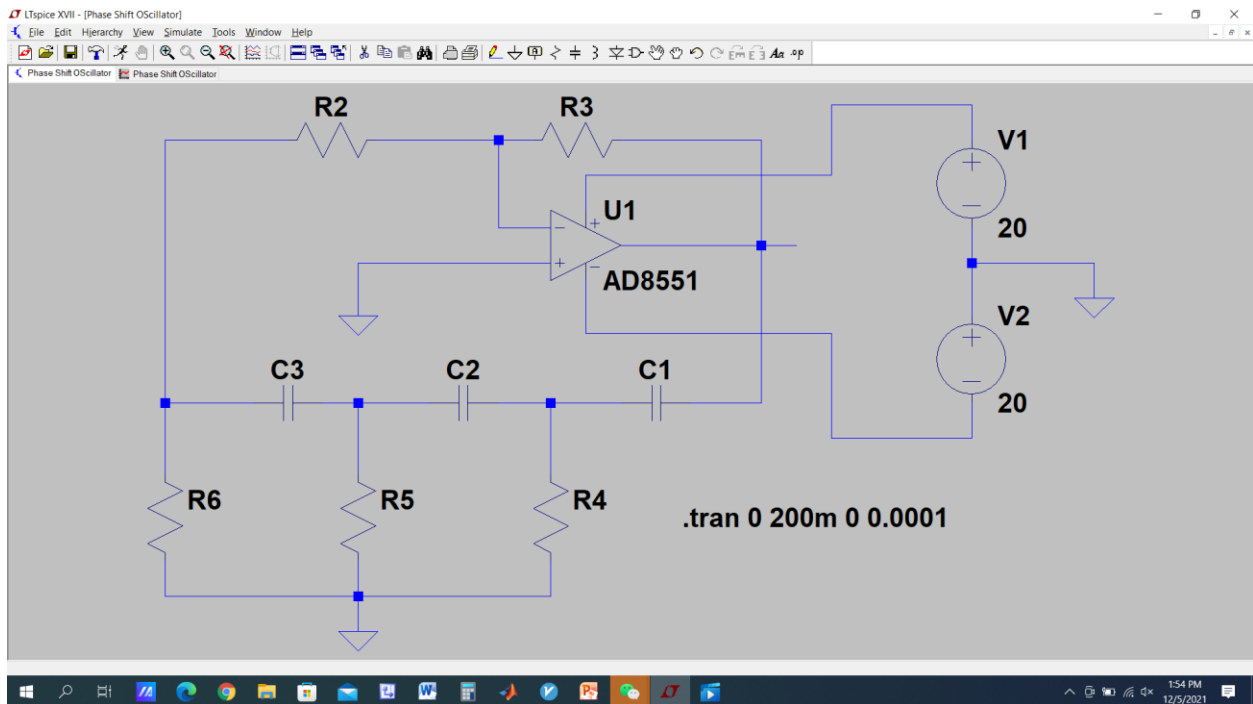- i. Mathematical Analysis
- ii. Simulate the circuit in LTSpice
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 20

### Group members:


王裕 Wang Yu 2019330308121

黄辰宇 Huang Chen Yu 2019330300108

Design and mathematically a quadrature oscillator generating a frequency of 350 kHz (Please refer to Lecture 8 (video lecture)).

The project report will be composed on the following steps

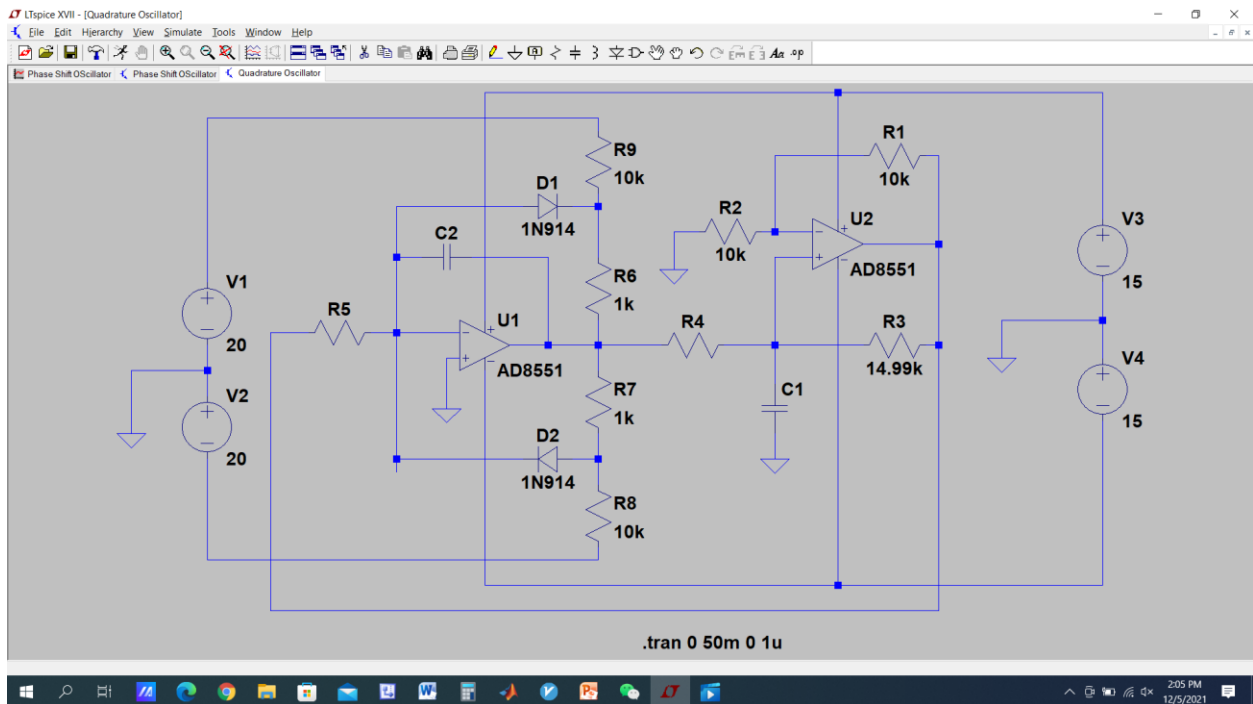- i. Mathematical Analysis
- ii. Simulate the circuit in LTSpice
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)


## Project # 21

Group members:

辛巩琦 Xing Gongqi 2019329600107

胥亦璇 Xu Yixuan 2019329600108

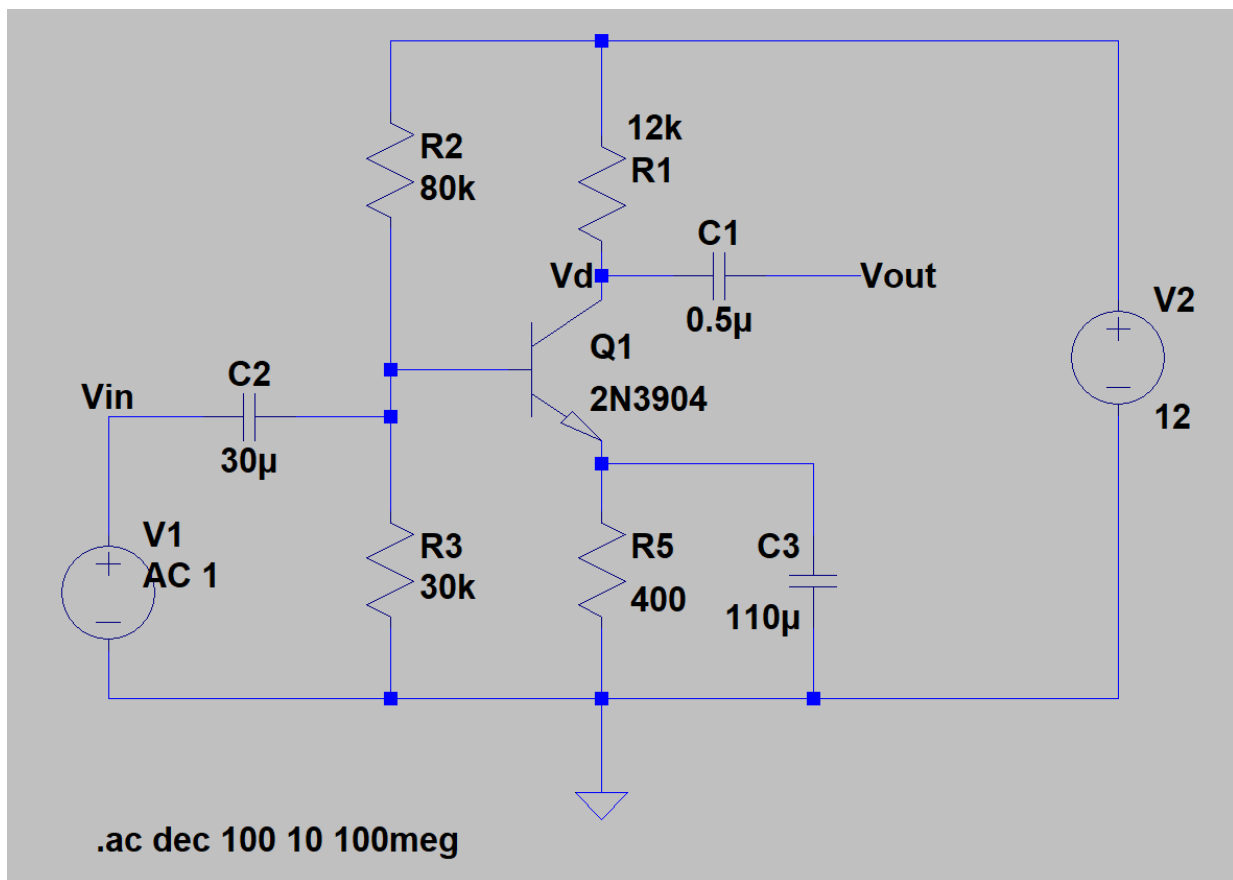- i. Do the Mathematical Analysis i.e. DC and Small signal analysis of the amplifier shown in figure and find the voltage gain (Reference class lecture #1)
- ii. Simulate the circuit in LTSpice and plot the Gain in dB and Linear scale, find the 3db bandwidth (Reference class lecture #1)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 22


Group members:

朱子安 Zhu Zia 2019329600058

曲 正 Qu Zheng 2019327130017

商梓言 Shang Ziyang 2019339900030

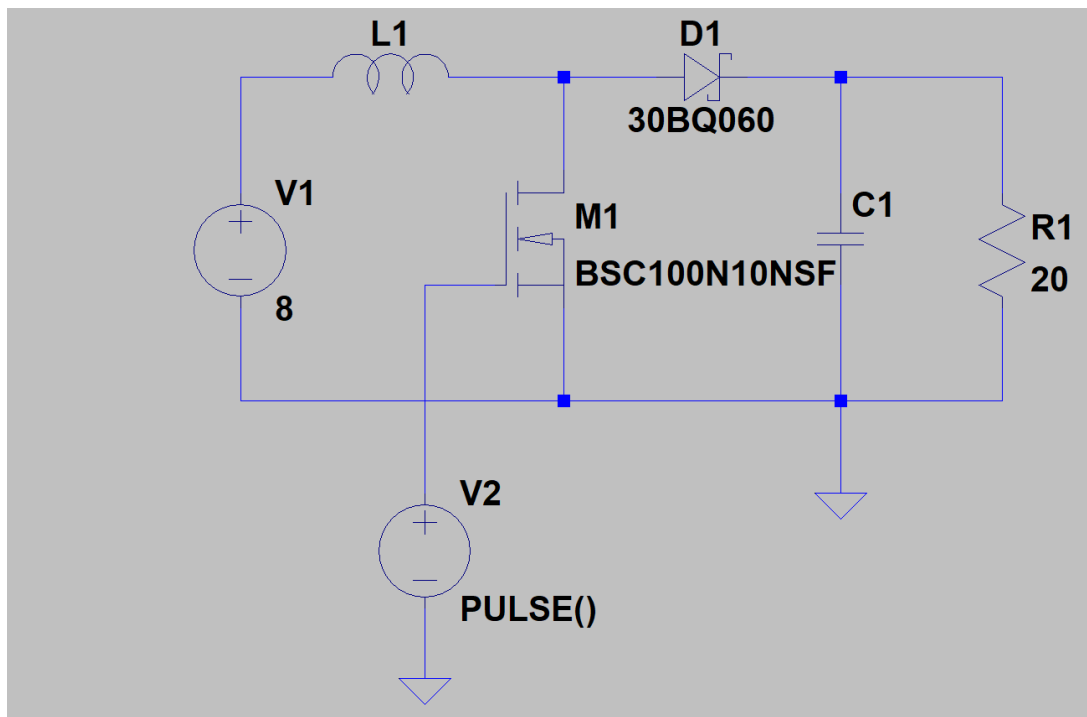- i. Design a boost converter that will have an output of 30 V from an 8V source. Design for continuous inductor current and an output ripple voltage of less than one percent. The load is a resistance of 20-Ohm. Assume ideal components for this design.
- ii. Simulate the circuit in LTSpice and plot the inductor current, capacitor current, output voltage and the switching signal(Reference class lecture #5 & 6)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)

## Project # 23


### Group members:

丛天昊 Cong Tianhao 2019329600065

陈晨 Chen Chen 2019329600063

胡涵嘉 Hu Hanjia 2019329600066

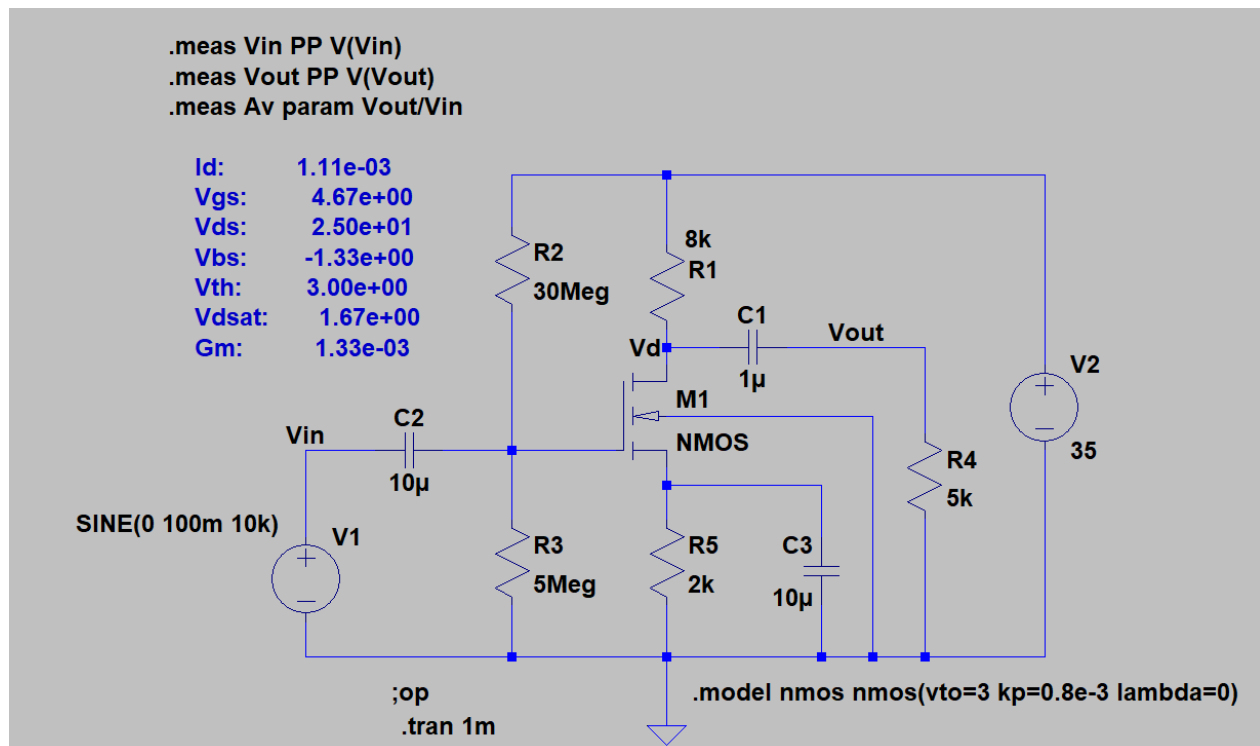- i. Do the Mathematical Analysis i.e. DC and Small signal analysis of the MOSFET amplifier shown in figure and find the voltage gain (Reference class lecture #2 & 3)
- ii. Simulate the circuit in LTSpice and plot the Gain in dB and Linear scale, find the 3db bandwidth (Reference class lecture #2 & 3)
- iii. Design the PCB of the amplifier using Altium Designer



Submit a report to the teacher composed of MS-word document (covering all the above three steps)